

# THE SERIAL CARAVAN

(Design and Verification of a UART Transmitter and Receiver System using Verilog HDL )

- **Category: Mid-Level Digital Design**

## Team Details:

- **Team Name: FMS Fours**

\*Divyansh Awasthi(20244066),phone no: 62619 68850  
Email id: divyansh.awasthi616@gmail.com


\* Arun kumar(20244038),phone no.:9772335423  
Email id:Arun.20244038@mnnit.ac.in

- **Branch/year: Electronics and Communication Engineering (ECE)/2<sup>nd</sup> year**

\*Anjaneer Kumar(20244021), phone no.:7607 613 093  
Email id: anjaneekumar76076@gmail.com

\*Krishna Mehrotra(20244096),phone no. :79058 44272  
Email id: Krishnamehrotra0406@gmail.com

# BLOCK DIAGRAM

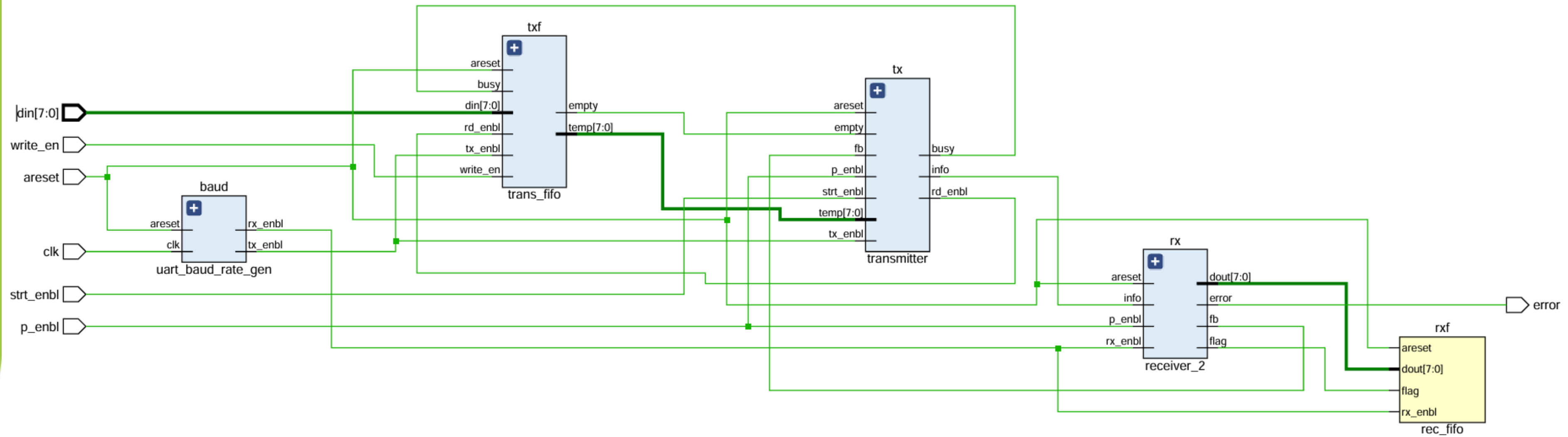

# Baud Rate Generator

- **module uart\_baud\_rate\_gen** //Defines the module name.
- **parameter integer CLK\_FREQ = 48000000** // Sets the default system clock to 48 MHz. Parameters allow you to reuse this code for different boards by just changing this value.
- **parameter integer BAUD\_RATE = 1000000**: Sets the target communication speed (1 Mbps).
- **input wire clk, areset**: The global system clock and an asynchronous reset (active high).
- **output reg tx\_enbl, rx\_enbl**: The generated clock signals. Note they are defined as reg because they are assigned inside an always block.
- **reg [\$clog2(TX\_DIV\_HALF)-1:0] tx\_cnt** //These are counters. The \$clog2 function automatically calculates the minimum number of bits needed to store the division value
- **TX\_DIV\_HALF**: Calculates how many clock cycles make up half a baud period ( $48,000,000 / 1,000,000 = 48$ ). Since the code toggles the output, the actual period will be  $48 \times 2 = 96$  cycles.

- **RX\_DIV\_HALF**: Calculates the cycles for the 16x faster clock ( $48,000,000 / (16 * 1,000,000) = 3$ ).
- **if (areset)**: When the reset signal goes high, everything is cleared to zero immediately, regardless of the clock. This ensures the system starts in a known state.
- **rx\_enbl** //It represents the clock signal used by the UART receiving logic to time the incoming serial data
- **if (tx\_cnt == TX\_DIV\_HALF - 1)**: The counter checks if it has reached the target number of cycles.
- **tx\_cnt <= 0**: Once reached, it resets the counter to start over.
- **tx\_enbl <= ~tx\_enbl**: This is the "Toggle." If the signal was 0, it becomes 1, and vice versa. By toggling every "half" period, it creates a perfect 50% duty cycle square wave at the target Baud Rate.

# UART Transmitter.

- **tx\_enbl**: The baud rate clock pulses that drive the timing of each bit
- **strt\_enbl**: A control pulse that triggers the start of a transmission.
- **p\_enbl**: Parity Enable. If high, a parity bit will be calculated and sent.
- **fb**: Feedback signal from the receiver (used to trigger a re-transmission if an error occurred).
- **empty**: A signal from the FIFO; if high, there is no data to send.
- **temp**: The 8-bit parallel data currently waiting to be sent.
- **info**: The Serial Output Pin. This is where the physical transmission happens.
- **busy**: Tells the rest of the system the transmitter is currently occupied
- **rd\_enbl**: The "Read Enable" sent to the FIFO to request the next byte
- **reg [1:0] ps, ns**; Present State and Next State registers for the FSM (Finite State Machine).
- **reg [3:0] count**; A counter used to track which bit (0 through 7, plus parity) is currently being shifted out.



## Transmitter FIFO (First-In-First-Out) :-

- **input wire tx\_enbl:** The clock source for the FIFO. It uses the Baud Rate clock to synchronize data movement with the transmitter.
- **input wire areset:** The asynchronous reset signal. When high, it clears the FIFO's pointers and status.
- **input wire write\_en:** The "Push" signal. When this is high, the data on the din bus is saved into the memory.
- **input wire [7:0] din:** The 8-bit parallel data input coming into the FIFO.
- **input wire rd\_enbl:** The "Pop" signal. This is controlled by the Transmitter. When the transmitter is ready for a new byte, it pulses this high to grab data from the FIFO
- **input wire busy:** A status signal from the transmitter indicating it is currently sending a byte.
- **output reg [7:0] temp:** The 8-bit output of the FIFO. This holds the byte that is currently being "read" and handed over to the transmitter.
- **output wire empty:** A status flag. It is high when the FIFO has no data left to send.
- **reg [7:0] mem [0:15];** This is the Memory Array. It consists of 16 "slots" (0 to 15), where each slot is 8 bits wide.
- **reg [3:0] rear\_ptr;** The Write Pointer (Tail). It points to the address where the next incoming byte from din will be stored.
- **reg [3:0] front\_ptr;** The Read Pointer (Head). It points to the address of the next byte that needs to be sent to the transmitter.
- **reg [4:0] count;** This tracks the Fill Level (depth).

# UART Receiver

- **input areset**,: The Asynchronous Reset. When this pin goes high, the receiver immediately clears all its internal memory and goes back to the idle state, regardless of what the clock is doing.
- **input p\_enbl**,: Parity Enable. This is a control signal.
- **input rx\_enbl**,: This is the Oversampling Clock (usually 16x the Baud Rate). This is the actual "heartbeat" used by the always block to time the sampling of the info line.
- **input info**:The serial input line (RX).
- **output dout**: The parallelized 8-bit data output.
- **output error**: High if parity is wrong or stop bit is missing.
- **output fb**: Feedback signal sent back to the transmitter to request re-send.
- **output flag**: Acts as a "Write Enable" for the FIFO memory.
- **reg [3:0] data\_cnt**: Tracks which bit we are receiving (Bit 0 to 7, then Bit 8 for parity).
- **reg [3:0] s\_cnt**: The oversampling counter. Since rx\_enbl is 16x the baud rate, we count to 16 to move from one bit to the next.
- **reg [7:0] temp**: A shift register that holds bits as they arrive.
- **reg prev\_p**: Stores the parity enable state to ensure logic remains consistent during a transaction

# Receiver FIFO (First-In-First-Out) buffer

- **input rx\_enbl:** The oversampling clock (used here to synchronize internal logic).
- **input areset:** The asynchronous reset to clear the buffer.
- **input flag:** This is the write enable. It comes from the receiver; when the receiver finishes a byte, it pulses this high to tell the FIFO to "save" the data.
- **input [7:0] dout:** The 8-bit data byte arriving from the receiver.
- **reg [7:0] mem [0:15];** This creates the actual memory array.
  - It is a 2D array: 16 rows deep, and each row is 8 bits (1 byte) wide.
  - This means this FIFO can hold up to 16 bytes of data at once
- **reg [3:0] rear\_ptr;** This is the Write Pointer
  - It is 4 bits wide ( $2^4 = 16$ ), which allows it to point to any index in the mem from 0 to 15.
  - It tracks the next empty slot where the next incoming byte should be stored.
- **reg [4:0] count;** This tracks the fill level of the FIFO.
  - It is 5 bits wide so it can represent values from 0 up to 16.
  - Why 5 bits? To distinguish between the FIFO being "Empty" (0) and "Full" (16). If it were only 4 bits, both 0 and 16 would look like 0000
- **integer i:**for clearing the memory block



# TOPMODULE

- **module topmodule(...):** Defines the start of the module.
- **input clk:** The master system clock (usually 50MHz or 100MHz)
- **input areset:** Asynchronous reset signal to initialize all internal registers to zero.
- **input strt\_enbl:** A control signal to trigger the transmitter to begin sending data.
- **input [7:0] din:** The 8-bit data input that you want to transmit.
- **input write\_en:** A signal that tells the transmit FIFO to "capture" the data on the din bus.
- **input p\_enbl:** Parity enable. If high, the system likely calculates a parity bit for error checking.
- **output error:** High if the receiver detects a mismatch in data or parity.
- **wire tx\_enbl, rx\_enbl:** Clock pulses from the baud generator to keep everything at the right speed.

- **wire info:** This is the most important wire. It is the single-bit serial line where data travels bit-by-bit from the transmitter to the receiver.
- **wire flag:** A signal from the receiver indicating a full byte has been successfully reconstructed.
- **wire [7:0] dout:** The 8-bit parallel data reconstructed by the receiver
- **wire rd\_enbl:** Handshaking signal; the transmitter uses this to ask the FIFO for more data.
- **wire [7:0] temp:** Holds the byte currently being transferred from the FIFO to the transmitter.
- **wire empty:** Status signal from the FIFO; if high, the transmitter knows there is no data left to send.
- **wire busy:** High when the transmitter is currently shifting bits and cannot accept new data.

```
fifo content      463670000
addr[ 0]: data=96
addr[ 1]: data=66
addr[ 2]: data=43
addr[ 3]: data=53
addr[ 4]: data=63
addr[ 5]: data=01
addr[ 6]: data=12
addr[ 7]: data=24
addr[ 8]: data=33
addr[ 9]: data=46
addr[10]: data=77
addr[11]: data=81
addr[12]: data=13
addr[13]: data=15
addr[14]: data=67
addr[15]: data=69
fifo content      479030000
addr[ 0]: data=69
addr[ 1]: data=96
addr[ 2]: data=66
addr[ 3]: data=43
addr[ 4]: data=53
addr[ 5]: data=63
addr[ 6]: data=01
addr[ 7]: data=12
addr[ 8]: data=24
addr[ 9]: data=33
addr[10]: data=46
addr[11]: data=77
addr[12]: data=81
addr[13]: data=13
addr[14]: data=15
addr[15]: data=67
```

- Reading contents of transmitter fifo memory block

- reading contents of receiver fifo memory block

```
fifo content          461750000
addr[ 0]: data=96
addr[ 1]: data=66
addr[ 2]: data=43
addr[ 3]: data=53
addr[ 4]: data=63
addr[ 5]: data=01
addr[ 6]: data=12
addr[ 7]: data=24
addr[ 8]: data=33
addr[ 9]: data=46
addr[10]: data=77
addr[11]: data=81
addr[12]: data=13
addr[13]: data=15
addr[14]: data=67
addr[15]: data=69
fifo content          477110000
addr[ 0]: data=00
addr[ 1]: data=96
addr[ 2]: data=66
addr[ 3]: data=43
addr[ 4]: data=53
addr[ 5]: data=63
addr[ 6]: data=01
addr[ 7]: data=12
addr[ 8]: data=24
addr[ 9]: data=33
addr[10]: data=46
addr[11]: data=77
addr[12]: data=81
addr[13]: data=13
addr[14]: data=15
addr[15]: data=67
$finish called at time : 477110 ns
```

- with feedback high at 77 ---> error was made high

Your paragraph text



# OUTPUT

